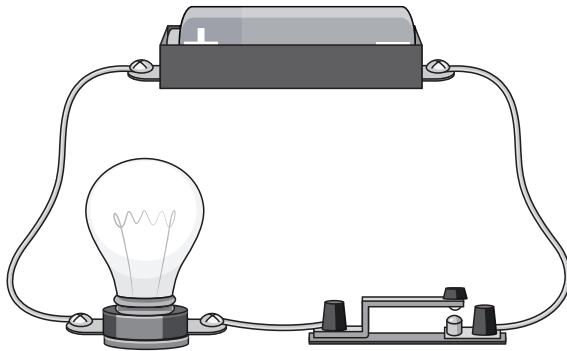


How Does Electricity Work?

1. What is electricity?

2. What three things does a circuit need?



3. What does a switch do in a circuit?

4. What makes good conductors and good insulators?

5. Build and Test a Mini Flashlight!

- Draw a plan of your flashlight showing: a battery, wires, a bulb (or LED), and a switch.

OR

- Build it using simple materials: wires, battery, bulb/LED, switch. For information on how to build a circuit visit:
https://www.ducksters.com/science/experiment_electronic_circuit.php